

## Electrical Circuits (2)

### Sheet 4 - Natural RLC parallel circuits

1. The circuit elements in the circuit in Fig. 1 are  $R = 200 \text{ ohm}$ ,  $C = 200 \text{ nF}$ , and  $L = 50 \text{ mH}$ . The initial inductor current is  $-45 \text{ mA}$ , and the initial capacitor voltage is  $15 \text{ V}$ .

a) Calculate the initial current in each branch of the circuit.

b) Find  $v(t)$  for  $t > 0$ .

c) Find  $i_L(t)$  for  $t > 0$ .

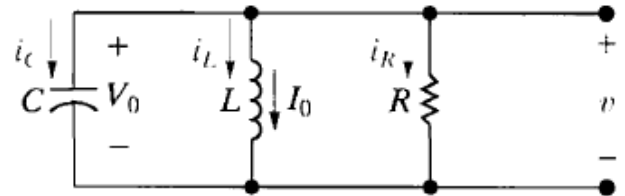


Fig. 1

2. The initial value of the voltage  $v$  in the circuit in Fig. 1 is zero, and the initial value of the capacitor current  $i_c(0^+)$ , is  $45 \text{ mA}$ . The expression for the capacitor current is known to be

$$i_c(t) = A_1 e^{-200t} + A_2 e^{-800t} \quad t > 0^+,$$

And  $R$  is  $250 \text{ ohm}$ . Find

- The values of  $\alpha$ ,  $\omega_0$ ,  $L$ ,  $C$ ,  $A_1$  and  $A_2$ .
- The expression for  $v(t)$ ,  $t \geq 0$ ,
- The expression for  $i_R(t) \geq 0$ ,
- The expression for  $i_L(t) \geq 0$ .

3. The two switches in the circuit seen in Fig.2 operate synchronously. When switch 1 is in position a, switch 2 is in position d. When switch 1 moves to position b, switch 2 moves to position c. Switch 1 has been in position a for a long time. At  $t = 0$ , the switches move to their alternate positions. Find  $v_o(t)$  for  $t \geq 0$ .

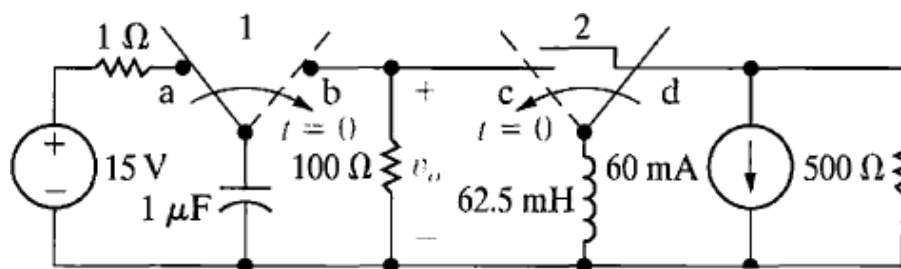


Fig. 2